## Al Muhit Muhtadi

## December 2023

## 1 Truth Table

cs2	cs1	cs0	$X_i$	$Y_i$	$Z_i$	$C_{in}$	Function
0	0	0	$A_i$	$B_i$	$C_i$	0	Add
0	0	1	$\bar{A}_i$	0	$C_i$	1	NEG A
0	1	0	$A_i$	$B_i$	$C_i$	0	Add
0	1	1	$A_i$	$B_i$	$C_i$	1	Add with carry
1	0	0	$A_i$	0	$C_i$	1	Increment A
1	0	1	$A_iB_i$	0	$C_i$	0	AND
1	1	0	$A_i \oplus B_i$	0	$C_i$	0	XOR
1	1	1	$A_i \oplus B_i$	0	$C_i$	0	XOR

Table 1: Truth Table of Intermediate  ${\rm I/O}$ 

cs2	cs1	cs0	$X_i$	$S_{x_1}$	$S_{x_0}$
0	0	0	$A_i$	0	0
0	0	1	$\bar{A}_i$	0	1
0	1	0	$A_i$	0	0
0	1	1	$A_i$	0	0
1	0	0	$A_i$	0	0
1	0	1	$A_iB_i$	1	1
1	1	0	$A_i \oplus B_i$	1	0
1	1	1	$A_i \oplus B_i$	1	0

Table 2: Truth Table of MUX input for  $X_i$ 

cs2	cs1	cs0	$X_i$	$S_{y_0}$
0	0	0	$\begin{bmatrix} B_i \\ 0 \end{bmatrix}$	0
0	0	1		1
0	1	0	$B_i$	0
0	1	1	$ \begin{vmatrix} B_i \\ B_i \\ 0 \end{vmatrix} $	0
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

Table 3: Truth Table of MUX input for  $Y_i$