

# 1 Block Diagram

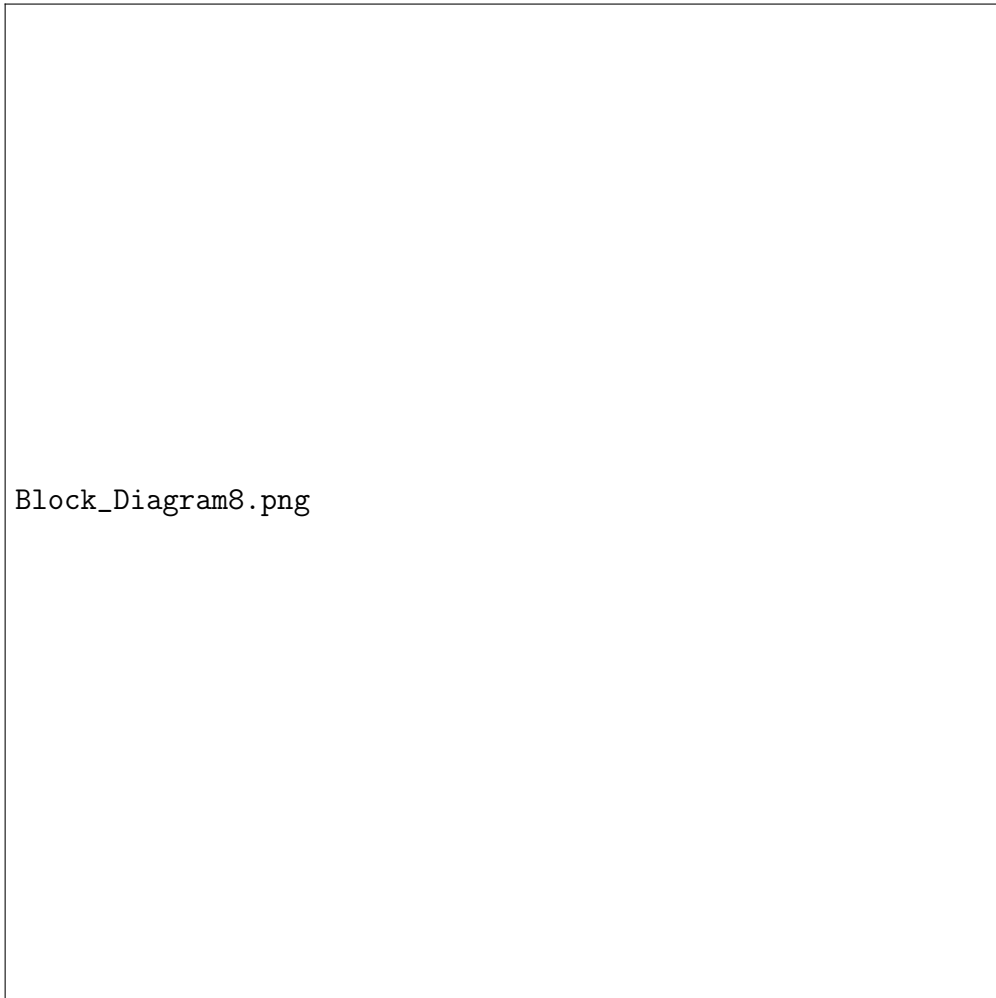


Figure 1: Block Diagram of ALU

## 2 Complete Circuit Diagram

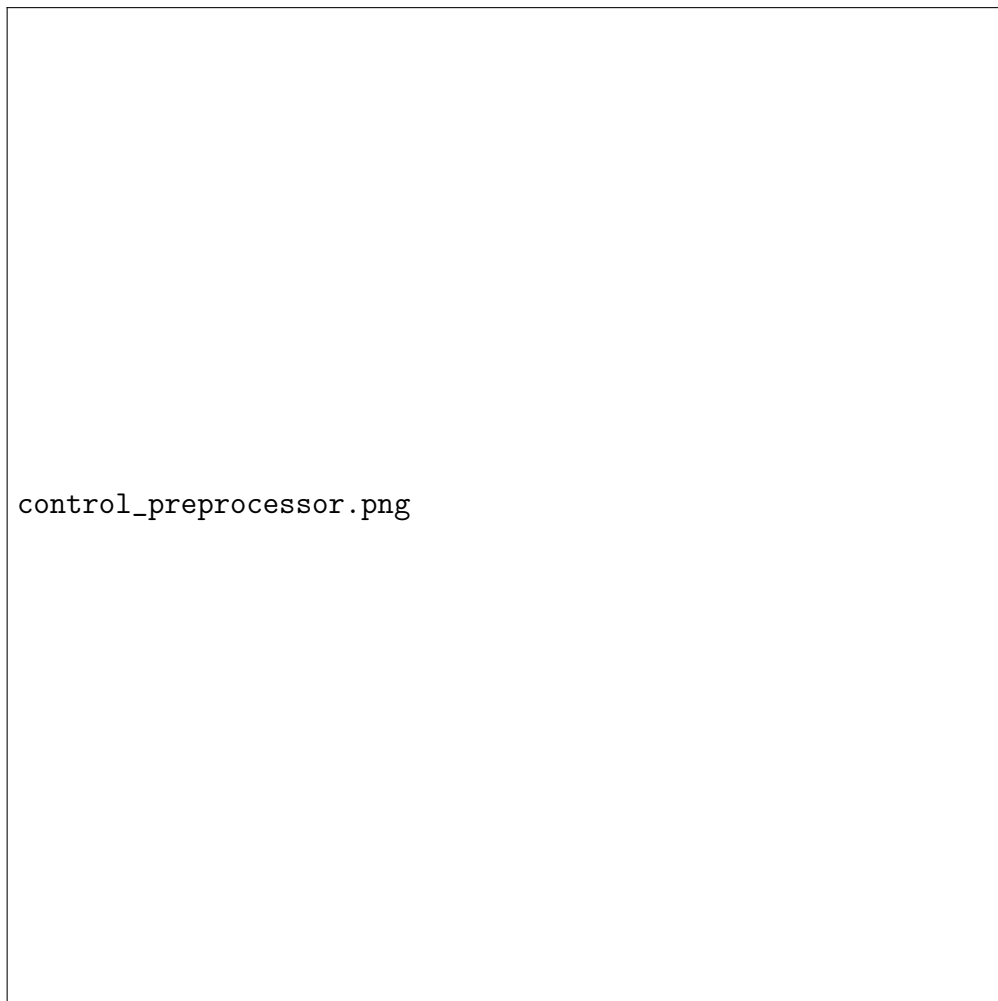


Figure 2: Control Processing Unit

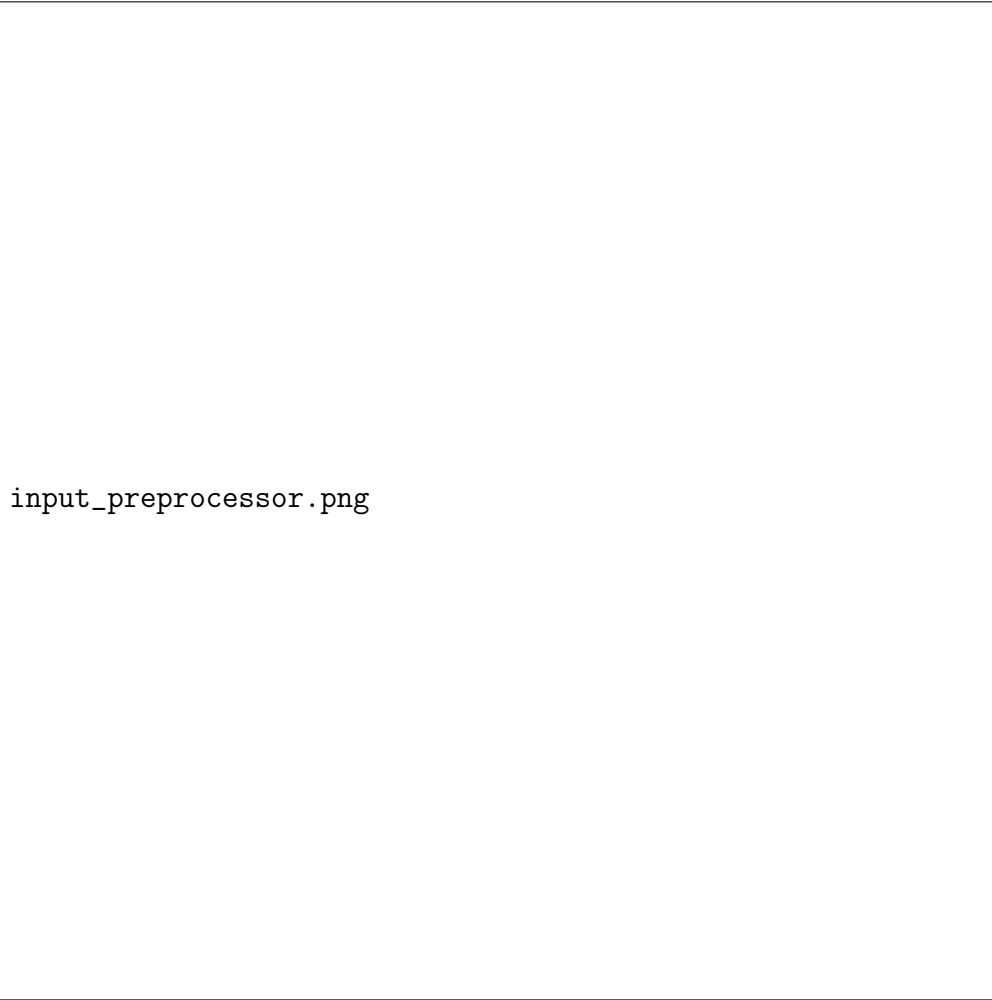


Figure 3: Input Processing Unit



Figure 4: The Alu